

# Science - Electricity

#### Component (parts) vocabulary

cell: Normally, we would call this a battery but scientifically, this is a cell. Two or more cells joined together form a battery.



wires: Used to connect the different components in the circuit together.



bulb: Lights up in a complete circuit.



motor: Produces movement in a complete circuit.



buzzer: Makes a noise in a complete circuit.



switch: Used to turn other components in the circuit on or off.



#### Electrical appliances

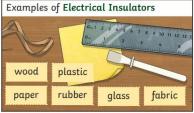
#### Appliances

Many everyday appliances rely on electricity for them to work. Some appliances use mains electricity (are plugged into a socket) and others have a battery to make them work. Examples of mains-powered appliances include toasters and televisions. Battery-powered appliances can include mobile phones and torches.









#### lectrical circuits


#### Series Circuit

A circuit where the components are connected in a loop.

Electricity flows through each component in a single pathway.



## Complete Circuit

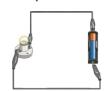

Electricity can flow.
The components
will work.

### Incomplete Circuit

There is a break in the circuit that prevents the electricity from flowing. The components will not work.



Switches can be used to open or close a circuit. When off, a switch 'breaks' the circuit to stop the flow of electricity. When on, a switch 'completes' the circuit and allows the electricity to flow.



push button switch



| Key Vocabulary            |  |
|---------------------------|--|
| Electricity               | The flow of an electric current though a material e.g. from a power source through wires to an appliance.  |
| Appliances                | A piece of equipment or a device designed to perform a particular job, such as a washing machine or mobile phone.  |
| Battery                   | A device that stores electrical energy as a chemical.  |
| <b>C</b> ircuit           | A pathway that electricity can flow around. It is based around wires and a power supply.<br>Examples of components (parts) you can add in to a circuit are bulbs, switches, buzzers<br>and motors. |
| <b>M</b> ains electricity | Electricity supplied through wires to a building.  |
| Electrical<br>conductor   | A conductor of electricity is a material that will allow electricity to flow through it.   |
| Electrical<br>insulator   | Materials that are electrical insulators do not allow electricity to flow through them.  |



## Electricity - Skills - Working Scientifically

## National Curriculum


Using straightforward scientific evidence to answer questions or to support their findings.

Using results to draw simple conclusions, make predictions for new values, suggest improvements and raise further questions.

Recording findings using simple scientific language, drawings, labelled diagrams, keys, bar charts, and tables.

Asking relevant questions and using different types of scientific enquiries to answer them.

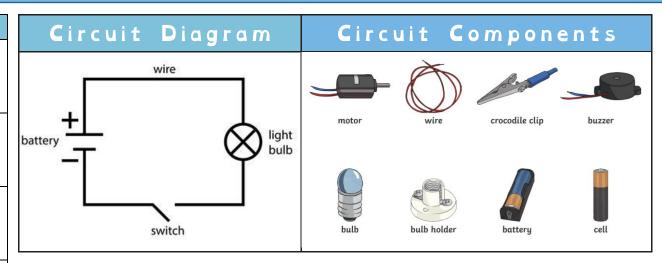Setting up simple practical enquiries, comparative and fair tests.



| Key Vocabulary |  |
|----------------|--|
| classify       | To arrange a group of people/organisms or things into classes or categories.                         |
| compare        | Note similarities and differences between different things e.g. compare different types of materials |
| diagram        | A drawn and annotated representation of how an experiment has been set up.                           |
| observation    | Spotting patterns and changes over time.   |
| data           | Information that has been collected.   |
| fair test      | A test that controls all but one variable when attempting to answer a scientific                     |
|                | question.  |